

Stabilizator serie cu reactie , configuratie Darlington



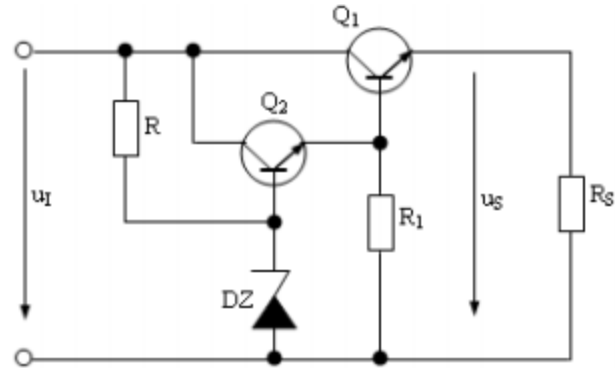


Fig. 9.14 Schema stabilizatorului serie cu reactie, fără amplificator de eroare cu montaj Darlington

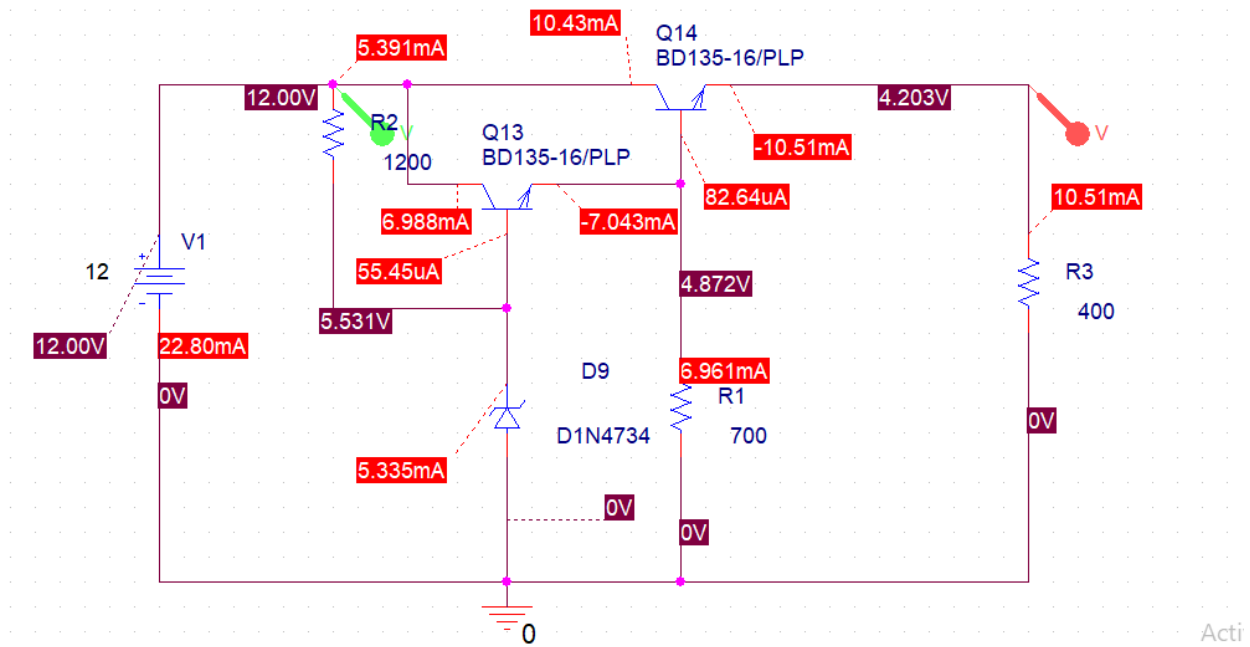

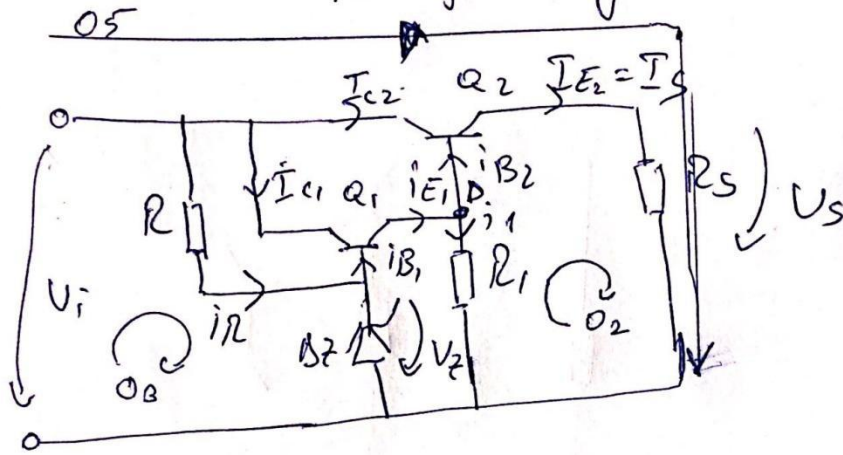Stabilizator serie cu reactiv Montaj Darlington



$$U_i = 12V$$

$$U_s = 5V$$

$$\beta_1 = \beta_2 = 100$$

$$R = 1,2 K\Omega$$

$$R_1 = 700\Omega$$

$$R_s = 400\Omega$$

$$K_{II}(01): V_{CC} - I_{R_2} R_2 - V_{BE1} - I_E R_s = 0$$

$$I_E = I_s = \beta_2 I_{B2} + I_{B2} = (\beta_2 + 1) I_{B2} \approx I_{B2} \beta_2$$

$$I_E = \beta_2 (I_{E1} - I_{R1}) = \beta_2 (\beta_1 I_{B1} - I_{R1})$$

$$K_{II}(1): I_{E1} = I_{B2} + I_{R1} \Rightarrow I_{B2} = I_{E1} - I_{R1}$$

$$I_{E1} = I_{B1} + I_{C1} = (\beta_1 + 1) I_{B1} \approx \beta_1 I_{B1}$$

$$I_E = \beta_2 I_{B2} = \beta_2 (\beta_1 I_{B1} - I_{R1})$$

$$I_E = I_K = 10,5 \text{ mA}$$

$$U_S = U_Z - 1,4 = 5,6 - 1,4 = 4,2 \text{ V}$$

$$I_S = \frac{U_S}{R_S} = \frac{4,2}{400} = 10,5 \text{ mA}$$

$$I_E = \beta_2 \beta_1 I_{B1} - \beta_2 I_{R1} = \beta_D I_{B1} - \beta_2 I_{R1}$$

$$\beta_D = 100 \cdot 100 = 10.000$$

$$10,5 \text{ mA} = 10.000 \cdot I_{B1} - 100 \cdot 7 \text{ mA}$$

$$\text{KII}(02): U_{BE} + U_S - R_1 I_{R1} \Rightarrow I_{R1} = \frac{U_{BE} + U_S}{R_1}$$

$$= \frac{4,2 + 0,7}{400} = 7 \text{ mA} \Rightarrow U_{R1} = 400 \cdot 0,007 = 2,8 \text{ V} \approx 5 \text{ V}$$

$$I_{B1} = \frac{10,5 \text{ mA} + 100 \cdot 7 \text{ mA}}{10.000} = 71,5 \mu\text{A}$$

$$\text{KII}(03): V_i - R I_R - U_Z = 0 \Rightarrow I_R = \frac{V_i - U_Z}{R}$$

$$= \frac{12 - 5,6}{1200} = 5,3 \text{ mA}$$

$$U_R = 6,4 \text{ V}$$

$$\text{KII}(04): -V_i + V_{CE1} + R_1 I_{R1} = 0$$

$$V_{CE1} = V_i - U_{R1} = 12 - 5 = 7 \text{ V}$$

$$\text{KII}(05): V_{CE0} = V_i - U_S = 12 - 4,2 = 7,8 \text{ V}$$

Conclusions:

- When input voltage U_i rises => output voltage U_s tend to increase
- The value of the output voltage depends on the zenner diode: $U_s = U_z - 1.4$
- Has a much greater current gain because of the Darlington configuration
- U_z is always constant